
 


Electronic Circuits /2/


Dr. Nidal ZAIDAN

CHAPTER /2/


DESIGN OF FET AMPLIFIERS

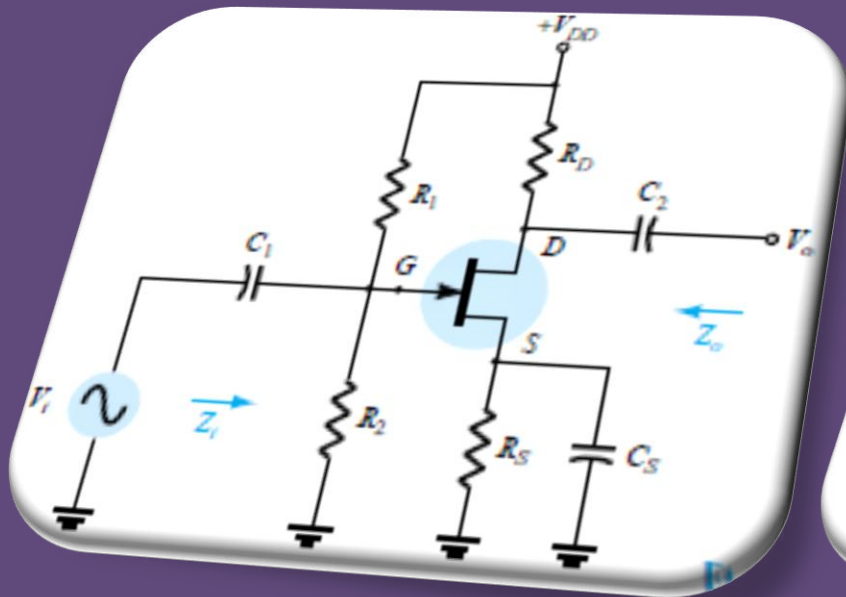

 
1. Basic Structure of The Two Type of JFET




(a) n channel

 



n channel

 


(b) p channel

 


n channel

  



2. Basic Structure of D-MOSFETS

 


(a) *n* channel

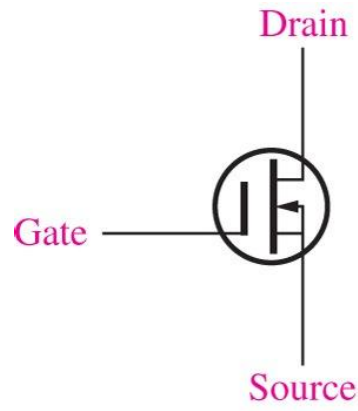


n channel

  







(b) *p* channel

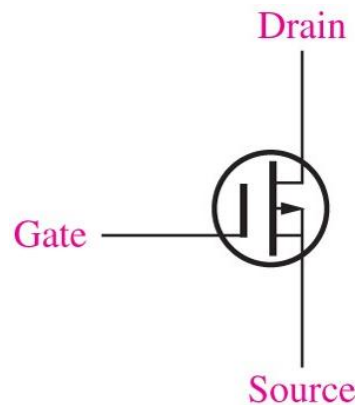

p channel

 

3. Basic Structure of E-MOSFETS

 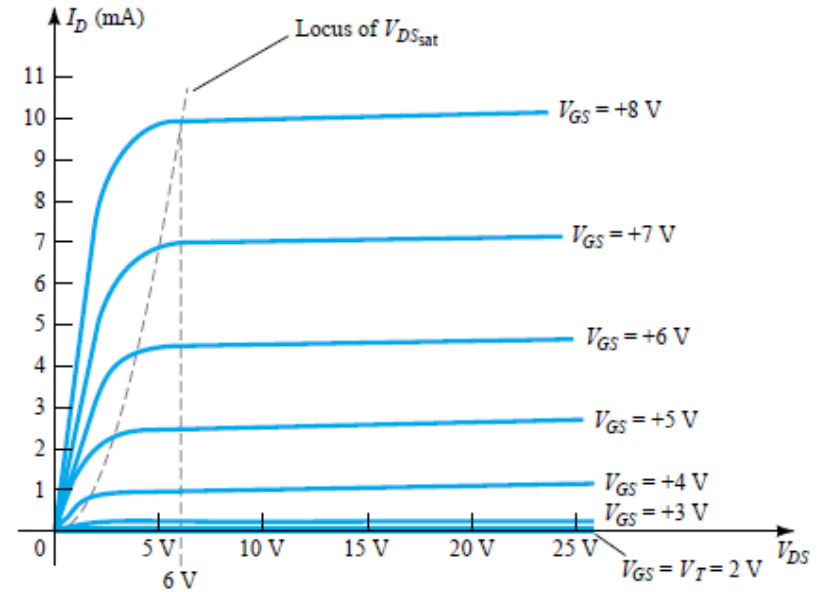   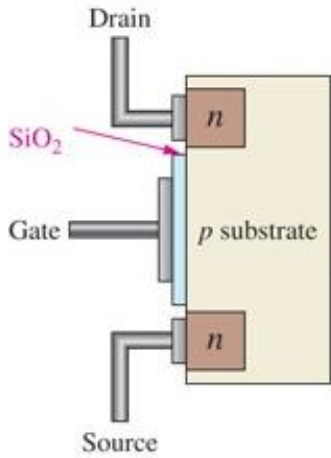

4. FET Biasing



For JFETs and depletion-type MOSFETs, Shockley's equation is applied to relate the input and output quantities



$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

For enhancement-type MOSFETs, the following equation is applicable

$$I_D = k(V_{GS} - V_T)^2$$

4.1. Fixed Bias Configuration

  


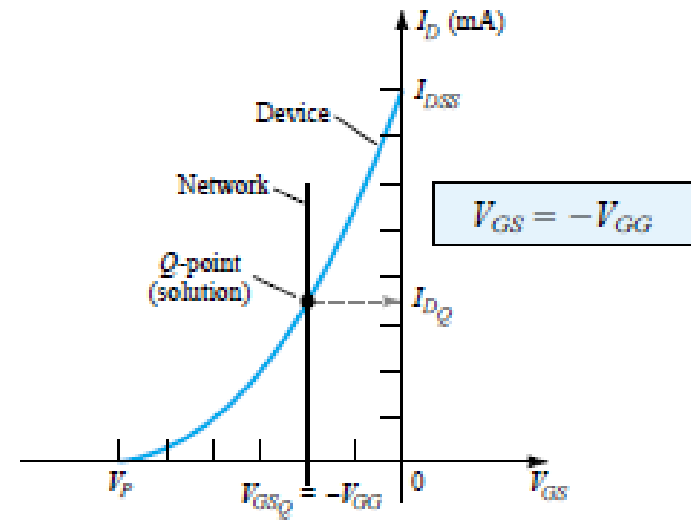 

 Example 1


Determine the following for the network

- V_{GSQ}
- I_{DQ}
- V_{DS}
- V_D
- V_G
- V_S




Solution

4.2. Self-Bias Configuration

 


$$V_{GS} = -I_D R_S$$

 

Example 2


Determine the following for the network

 - (a) V_{GS_Q} .
- (b) I_{D_Q} .
- (c) V_{DS} .
- (d) V_S .
- (e) V_G .
- (f) V_D .



Solution

4.3. Voltage-Divider Biasing

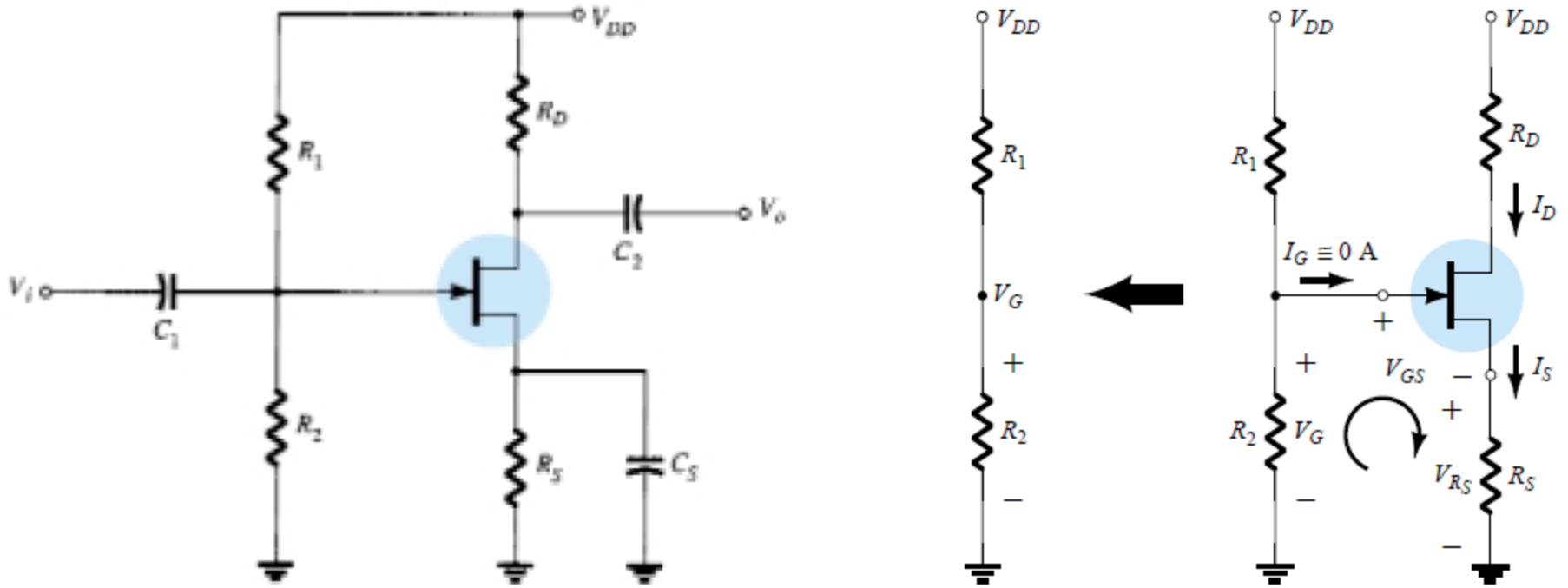


$$V_{GS} = V_G - I_D R_S$$

Example 3

Determine the following for the network

 - (a) I_{DQ} and V_{GSQ} .
- (b) V_D .
- (c) V_S .
- (d) V_{DS} .
- (e) V_{DG} .



Solution

5. FET Small Signal Model

The gate-to-source voltage controls the drain-to-source (channel) current of an FET

$$\Delta I_D = g_m \Delta V_{GS}$$



$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

$$g_m = m = \frac{\Delta y}{\Delta x} = \frac{\Delta I_D}{\Delta V_{GS}}$$

$$(a) \quad g_m = \frac{\Delta I_D}{\Delta V_{GS}} \cong \frac{2.1 \text{ mA}}{0.6 \text{ V}} = 3.5 \text{ mS}$$

$$(b) \quad g_m = \frac{\Delta I_D}{\Delta V_{GS}} \cong \frac{1.8 \text{ mA}}{0.7 \text{ V}} \cong 2.57 \text{ mS}$$
  
$$(c) \quad g_m = \frac{\Delta I_D}{\Delta V_{GS}} = \frac{1.5 \text{ mA}}{1.0 \text{ V}} = 1.5 \text{ mS}$$



Mathematical Definition of g_m

If we therefore take the derivative of I_D with respect to V_{GS} (differential calculus) using Shockley's equation, an equation for g_m can be derived as follows:

$$\begin{aligned}g_m &= \left. \frac{\Delta I_D}{\Delta V_{GS}} \right|_{Q\text{-pt.}} = \left. \frac{dI_D}{dV_{GS}} \right|_{Q\text{-pt.}} = \frac{d}{dV_{GS}} \left[I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \right] \\&= I_{DSS} \frac{d}{dV_{GS}} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = 2I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right] \frac{d}{dV_{GS}} \left(1 - \frac{V_{GS}}{V_P} \right) \\&= 2I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right] \left[\frac{d}{dV_{GS}} (1) - \frac{1}{V_P} \frac{dV_{GS}}{dV_{GS}} \right] = 2I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right] \left[0 - \frac{1}{V_P} \right]\end{aligned}$$

and

$$g_m = \frac{2I_{DSS}}{|V_P|} \left[1 - \frac{V_{GS}}{V_P} \right]$$

$$V_{GS} = 0 \text{ V.} \quad \longrightarrow \quad g_m = \frac{2I_{DSS}}{|V_P|} \left[1 - \frac{0}{V_P} \right]$$

$$g_{m0} = \frac{2I_{DSS}}{|V_P|}$$

$$g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_P} \right) = g_{m0} \sqrt{\frac{I_D}{I_{DSS}}}$$



FET Input Impedance Z_i

$$Z_i (\text{FET}) = \infty \Omega$$


FET Output Impedance Z_o

$$Z_o (\text{FET}) = r_d = \frac{1}{y_{os}}$$

$$r_d = \left. \frac{\Delta V_{DS}}{\Delta I_D} \right|_{V_{GS}=\text{constant}}$$

  

FET AC Equivalent Circuit


 



EXAMPLE

Given $y_{fs} = 3.8 \text{ mS}$ and $y_{os} = 20 \text{ } \mu\text{S}$, sketch the FET ac equivalent model.

Solution


5.1. JFET Fixed Bias Configuration

  

 

$$Z_i = R_G$$

 Z_o : Setting $V_i = 0$ V as required by the definition of Z_o will establish V_{gs} as 0 V also. The result is $g_m V_{gs} = 0$ mA, and the current source can be replaced by an open-circuit equivalent as shown in Fig. 9.13. The output impedance is



$$Z_o = R_D \parallel r_d$$

$$V_o = -g_m V_{gs} (r_d \parallel R_D)$$

but

$$V_{gs} = V_i$$

and

$$V_o = -g_m V_i (r_d \parallel R_D)$$

so that

$$A_v = \frac{V_o}{V_i} = -g_m (r_d \parallel R_D)$$

If $r_d \geq 10R_D$:


$$A_v = \frac{V_o}{V_i} = -g_m R_D$$

$r_d \geq 10R_D$

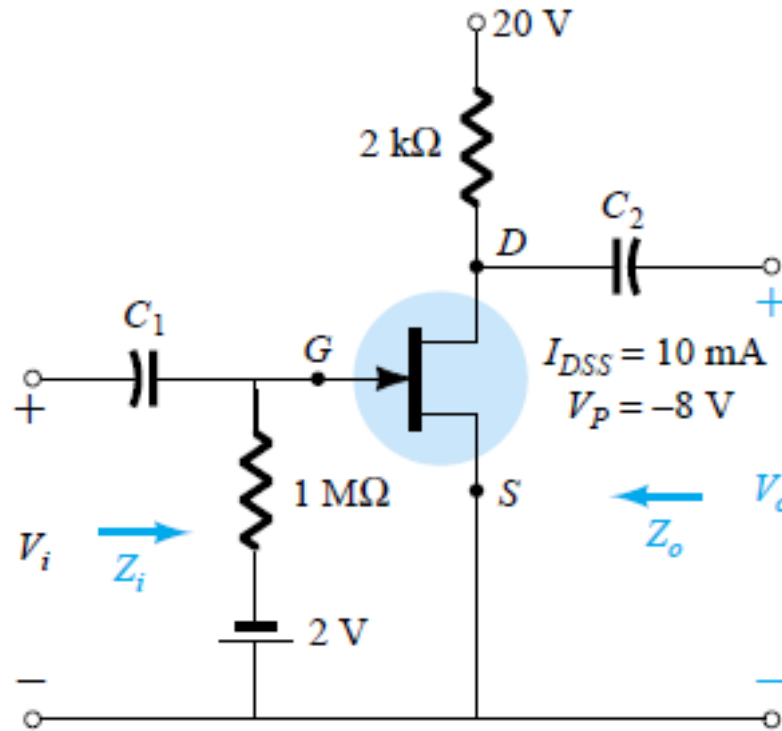Example 4



The fixed-bias configuration of Example 1 had an operating point defined by $V_{GS_Q} = -2\text{ V}$ and $I_{D_Q} = 5.625\text{ mA}$, with $I_{DSS} = 10\text{ mA}$ and $V_P = -8\text{ V}$. The network is redrawn as Fig. 9.14 with an applied signal V_i . The value of y_{os} is provided as $40\text{ }\mu\text{S}$.


- Determine g_m .
- Find r_d .
- Determine Z_i .
- Calculate Z_o .
- Determine the voltage gain A_v .
- Determine A_v ignoring the effects of r_d .



Solution

5.2. JFET Self-Bias Configuration

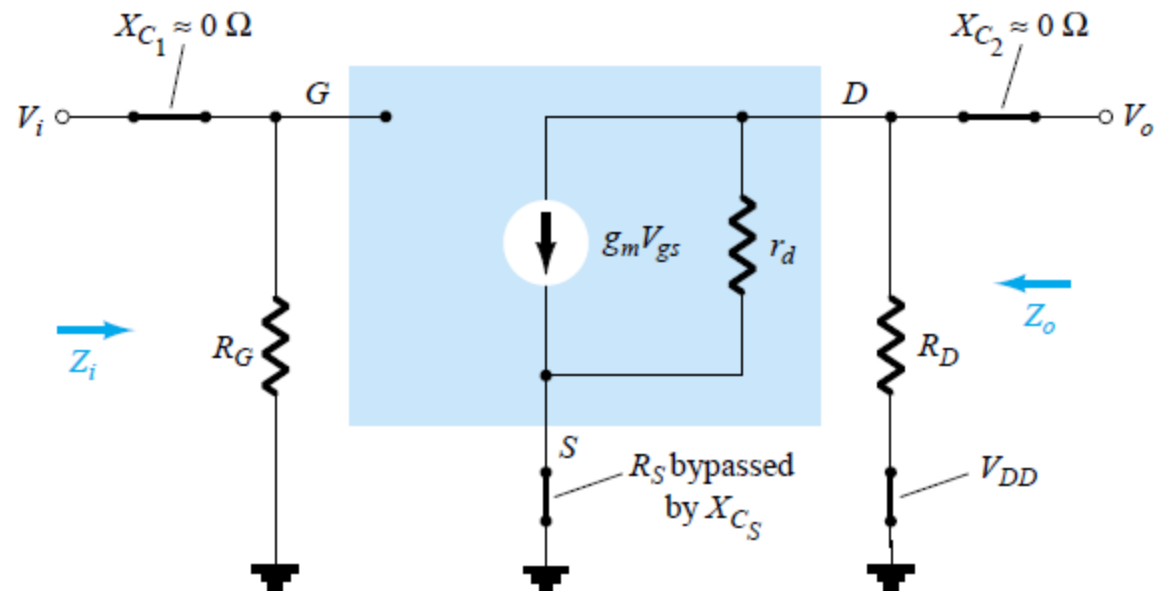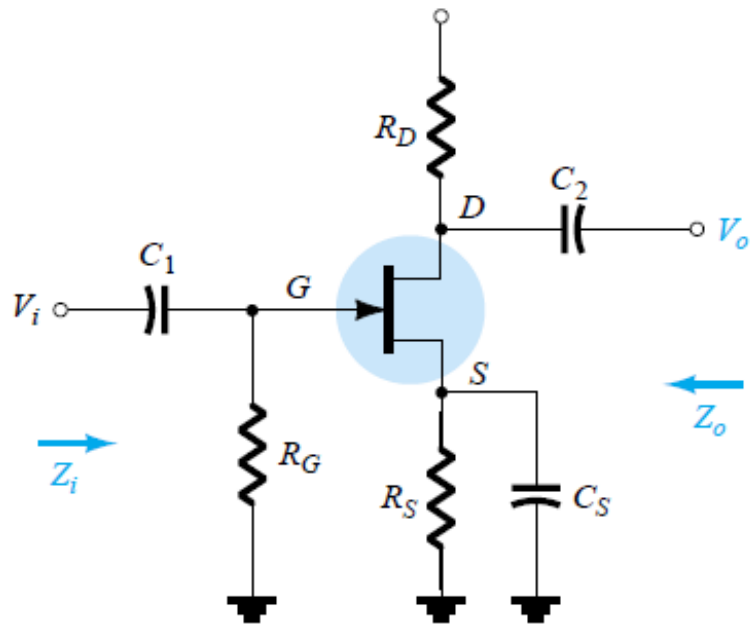

 

Z_i :

$$Z_i = R_G$$

Z_o :

$$Z_o = r_d \parallel R_D$$

If $r_d \geq 10R_D$,

$$Z_o \cong R_D \quad r_d \geq 10R_D$$


A_v :

$$A_v = -g_m(r_d \parallel R_D)$$

If $r_d \geq 10R_D$,

$$A_v = -g_m R_D \quad r_d \geq 10R_D$$

Unbypassed R_s

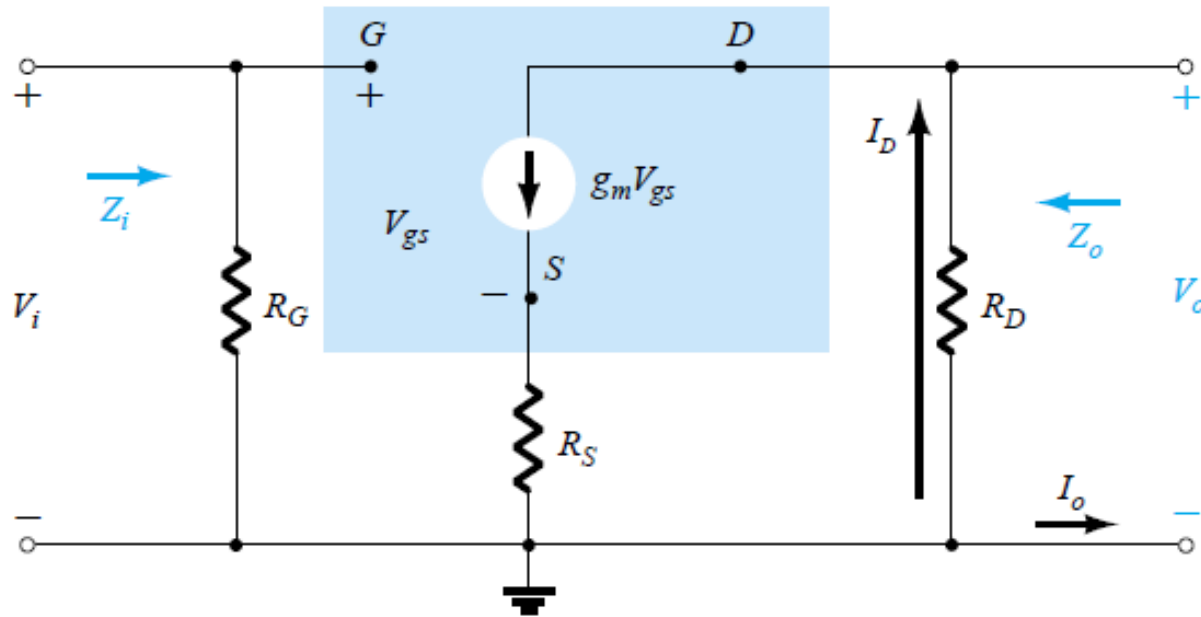

Z_i : Due to the open-circuit condition between the gate and output network, the input remains the following:

$$Z_i = R_G$$

(9.23)

Z_o : The output impedance is defined by

$$Z_o = \left. \frac{V_o}{I_o} \right|_{V_i = 0}$$

Applying Kirchhoff's current law will result in:

$$I_o + I_D = g_m V_{gs}$$

with

$$V_{gs} = -(I_o + I_D)R_S$$

so that

$$I_o + I_D = -g_m (I_o + I_D)R_S = -g_m I_o R_S - g_m I_D R_S$$

or

$$I_o[1 + g_m R_S] = -I_D[1 + g_m R_S]$$

and

$$I_o = -I_D \quad (\text{the controlled current source } g_m V_{gs} = 0 \text{ A for the applied conditions})$$

Since

$$V_o = -I_D R_D$$


then

$$V_o = -(-I_o)R_D = I_o R_D$$

and

$$Z_o = \frac{V_o}{I_o} = R_D \quad r_d = \infty \Omega$$

If r_d is included in the network

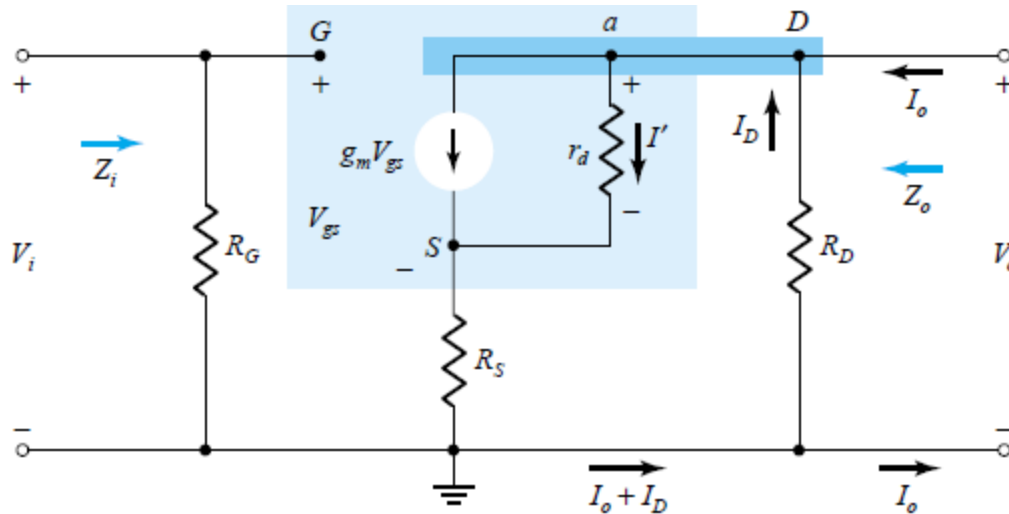

Since

$$Z_o = \left. \frac{V_o}{I_o} \right|_{V_i = 0 \text{ V}} = -\frac{I_D R_D}{I_o}$$

we should try to find an expression for I_o in terms of I_D .

Applying Kirchhoff's current law:

$$I_o = g_m V_{gs} + I_{r_d} - I_D$$

but

$$V_{r_d} = V_o + V_{gs}$$

and

$$I_o = g_m V_{gs} + \frac{V_o + V_{gs}}{r_d} - I_D$$

or

$$I_o = \left(g_m + \frac{1}{r_d} \right) V_{gs} - \frac{I_D R_D}{r_d} - I_D \text{ using } V_o = -I_D R_D$$

Now,

$$V_{gs} = -(I_D + I_o) R_S$$

so that

$$I_o = -\left(g_m + \frac{1}{r_d}\right)(I_D + I_o) R_S - \frac{I_D R_D}{r_d} - I_D$$

with the result that

$$I_o \left[1 + g_m R_S + \frac{R_S}{r_d} \right] = -I_D \left[1 + g_m R_S + \frac{R_S}{r_d} + \frac{R_D}{r_d} \right]$$

or

$$I_o = \frac{-I_D \left[1 + g_m R_S + \frac{R_S}{r_d} + \frac{R_D}{r_d} \right]}{1 + g_m R_S + \frac{R_S}{r_d}}$$

and

$$Z_o = \frac{V_o}{I_o} = \frac{-I_D R_D}{-I_D \left(1 + g_m R_S + \frac{R_S}{r_d} + \frac{R_D}{r_d} \right)} \cdot \frac{1 + g_m R_S + \frac{R_S}{r_d}}{1 + g_m R_S + \frac{R_S}{r_d}}$$

and finally,

$$Z_o = \frac{\left[1 + g_m R_S + \frac{R_S}{r_d} \right]}{\left[1 + g_m R_S + \frac{R_S}{r_d} + \frac{R_D}{r_d} \right]} R_D$$

For $r_d \geq 10 R_D$, $\left(1 + g_m R_S + \frac{R_S}{r_d}\right) \gg \frac{R_D}{r_d}$ and $1 + g_m R_S + \frac{R_S}{r_d} + \frac{R_D}{r_d}$
 $\cong 1 + g_m R_S + \frac{R_S}{r_d}$ and

$$\boxed{Z_o = R_D} \quad r_d \geq 10R_D$$

A_v : For the network of Fig. 9.19, an application of Kirchhoff's voltage law on the input circuit will result in

$$V_i - V_{gs} - V_{R_S} = 0$$

$$V_{gs} = V_i - I_D R_S$$

The voltage across r_d using Kirchhoff's voltage law is

$$V_o - V_{R_S}$$

and

$$I' = \frac{V_o - V_{R_S}}{r_d}$$

so that an application of Kirchhoff's current law will result in

$$I_D = g_m V_{gs} + \frac{V_o - V_{R_S}}{r_d}$$

Substituting for V_{gs} from above and substituting for V_o and V_{R_S} we have

$$I_D = g_m[V_i - I_D R_S] + \frac{(-I_D R_D) - (I_D R_S)}{r_d}$$

so that

$$I_D \left[1 + g_m R_S + \frac{R_D + R_S}{r_d} \right] = g_m V_i$$

or

$$I_D = \frac{g_m V_i}{1 + g_m R_S + \frac{R_D + R_S}{r_d}}$$

The output voltage is then

$$V_o = -I_D R_D = - \frac{g_m R_D V_i}{1 + g_m R_S + \frac{R_D + R_S}{r_d}}$$


and

$$A_v = \frac{V_o}{V_i} = - \frac{g_m R_D}{1 + g_m R_S + \frac{R_D + R_S}{r_d}}$$

 Example 5



The self-bias configuration of Example 2 has an operating point defined by $V_{GS_Q} = -2.6$ V and $I_{D_Q} = 2.6$ mA, with $I_{DSS} = 8$ mA and $V_P = -6$ V. The network is redrawn as Fig. 9.20 with an applied signal V_i . The value of y_{os} is given as 20 μ S.


- Determine g_m .
- Find r_d .
- Find Z_i .
- Calculate Z_o with and without the effects of r_d . Compare the results.
- Calculate A_v with and without the effects of r_d . Compare the results.



Solution

5.3. JFET Voltage-Divider Configuration

 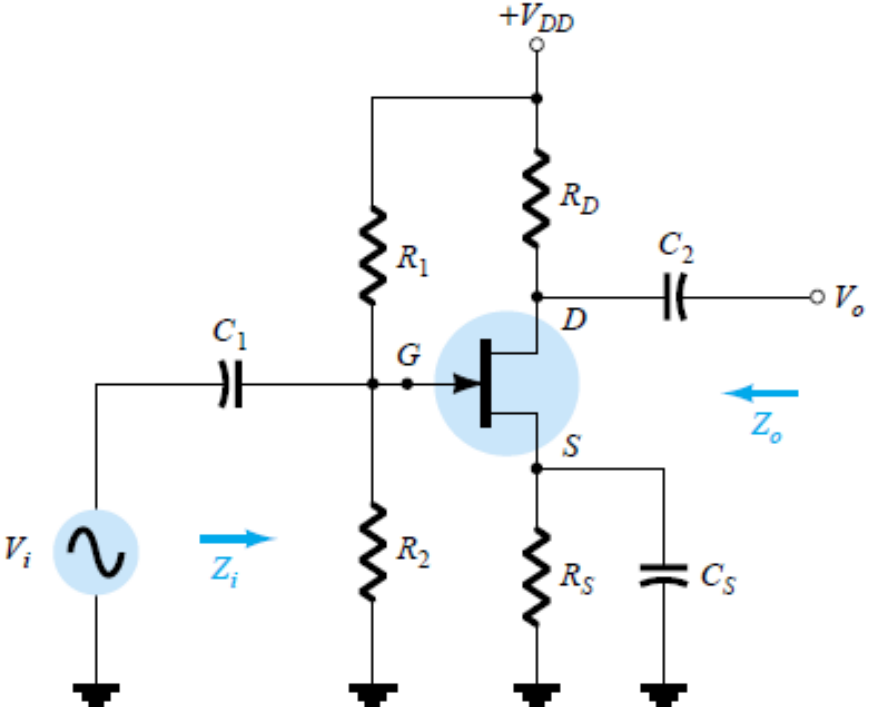

 

Z_i : R_1 and R_2 are in parallel with the open-circuit equivalence of the JFET resulting in

$$Z_i = R_1 \parallel R_2$$

Z_o : Setting $V_i = 0$ V will set V_{gs} and $g_m V_{gs}$ to zero and

$$Z_o = r_d \parallel R_D$$

For $r_d \geq 10R_D$,

$$Z_o \cong R_D$$

$r_d \geq 10R_D$

A_v :

$$V_{gs} = V_i$$

and

$$V_o = -g_m V_{gs} (r_d \parallel R_D)$$

so that

$$A_v = \frac{V_o}{V_i} = \frac{-g_m V_{gs} (r_d \parallel R_D)}{V_{gs}}$$

and

$$A_v = \frac{V_o}{V_i} = -g_m (r_d \parallel R_D)$$


If $r_d \geq 10R_D$,


$$A_v = \frac{V_o}{V_i} \cong -g_m R_D$$

$r_d \geq 10R_D$

Note that the equations for Z_o and A_v are the same as obtained for the fixed-bias and self-bias (with bypassed R_S) configurations. The only difference is the equation for Z_i , which is now sensitive to the parallel combination of R_1 and R_2 .

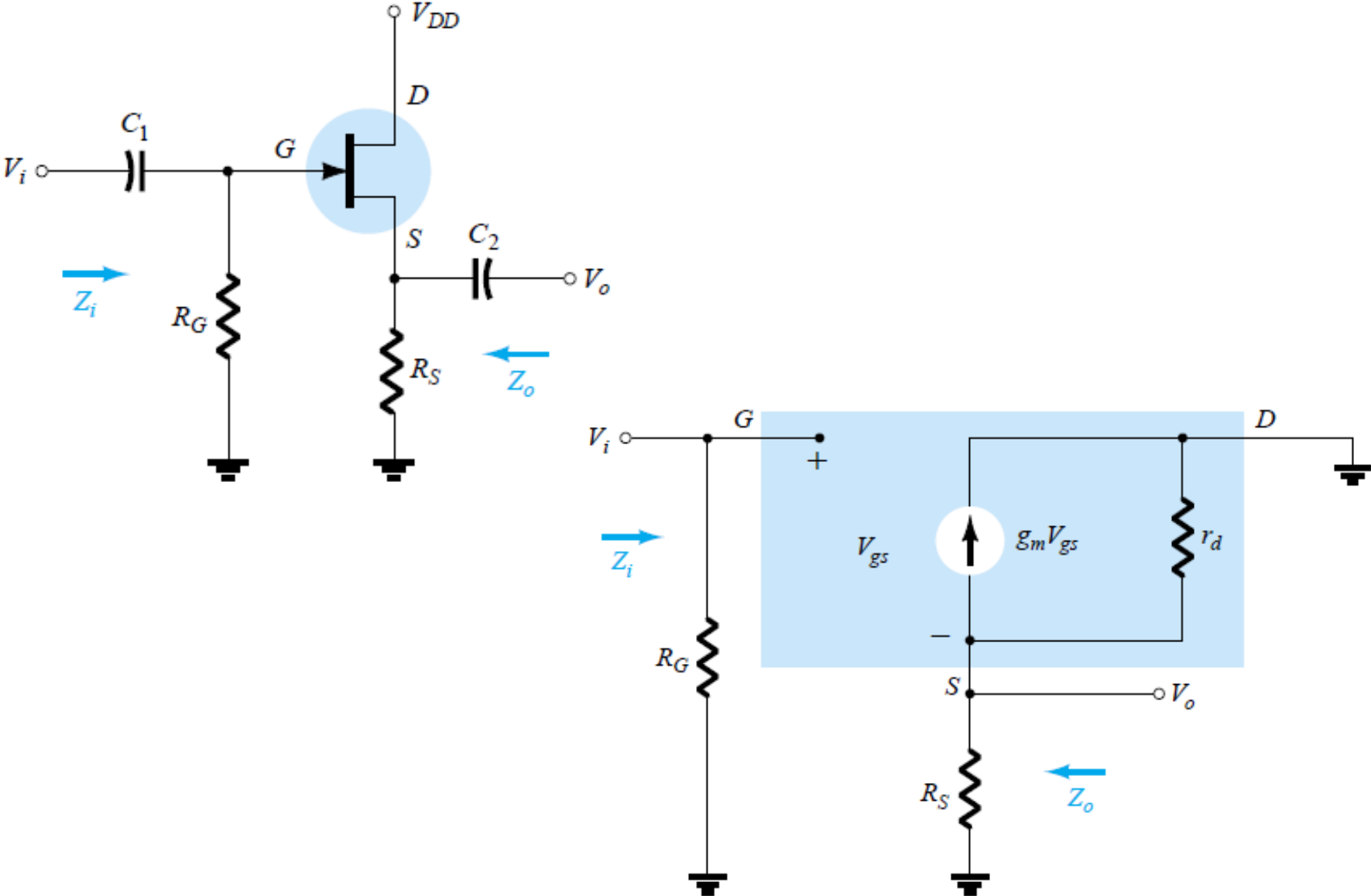
5.4. JFET Source Follower (Common-Drain) Configuration



 

Z_o : Setting $V_i = 0$ V will result in the gate terminal being connected directly to ground

 The fact that V_{gs} and V_o are across the same parallel network results in $V_o = -V_{gs}$.



Applying Kirchhoff's current law at node s ,

$$\begin{aligned} I_o + g_m V_{gs} &= I_{r_d} + I_{R_S} \\ &= \frac{V_o}{r_d} + \frac{V_o}{R_S} \end{aligned}$$

The result is

$$\begin{aligned} I_o &= V_o \left[\frac{1}{r_d} + \frac{1}{R_S} \right] - g_m V_{gs} \\ &= V_o \left[\frac{1}{r_d} + \frac{1}{R_S} \right] - g_m [-V_o] \\ &= V_o \left[\frac{1}{r_d} + \frac{1}{R_S} + g_m \right] \end{aligned}$$

$$\text{and } Z_o = \frac{V_o}{I_o} = \frac{V_o}{V_o \left[\frac{1}{r_d} + \frac{1}{R_S} + g_m \right]} = \frac{1}{\frac{1}{r_d} + \frac{1}{R_S} + g_m} = \frac{1}{\frac{1}{r_d} + \frac{1}{R_S} + \frac{1}{1/g_m}}$$

which has the same format as the total resistance of three parallel resistors. Therefore,

$$Z_o = r_d \parallel R_S \parallel 1/g_m$$

A_v : The output voltage V_o is determined by

$$V_o = g_m V_{gs} (r_d \parallel R_S)$$

and applying Kirchhoff's voltage law around the perimeter of the network will result in

$$V_i = V_{gs} + V_o$$

and

$$V_{gs} = V_i - V_o$$

so that

$$V_o = g_m (V_i - V_o) (r_d \parallel R_S)$$

or

$$V_o = g_m V_i (r_d \parallel R_S) - g_m V_o (r_d \parallel R_S)$$

and

$$V_o [1 + g_m (r_d \parallel R_S)] = g_m V_i (r_d \parallel R_S)$$

so that

$$A_v = \frac{V_o}{V_i} = \frac{g_m (r_d \parallel R_S)}{1 + g_m (r_d \parallel R_S)}$$

In the absence of r_d or if $r_d \geq 10R_S$,


$$A_v = \frac{V_o}{V_i} \cong \frac{g_m R_S}{1 + g_m R_S}$$

$r_d \geq 10R_S$

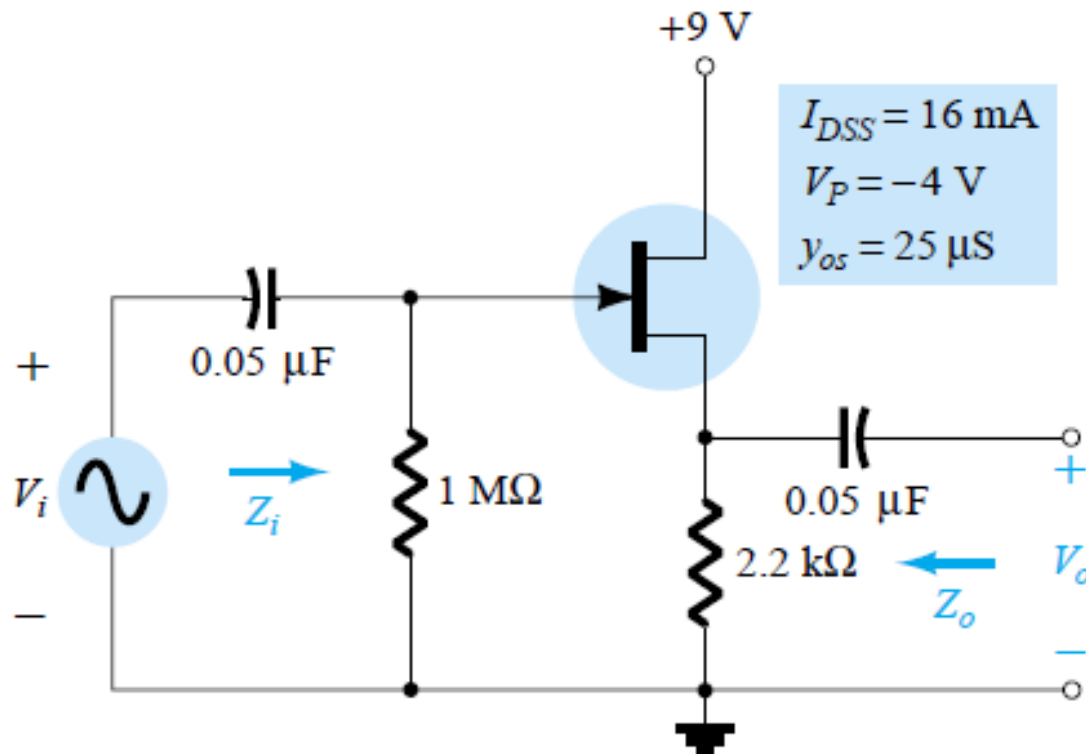Example 6



A dc analysis of the source-follower network will result in $V_{GS_Q} = -2.86$ V and $I_{D_Q} = 4.56$ mA.

- Determining g_m .
- Find r_d .
- Determine Z_i .
- Calculate Z_o with and without r_d . Compare results.
- Determine A_v with and without r_d . Compare results.




Solution

5.5. JFET Common-Gate Configuration

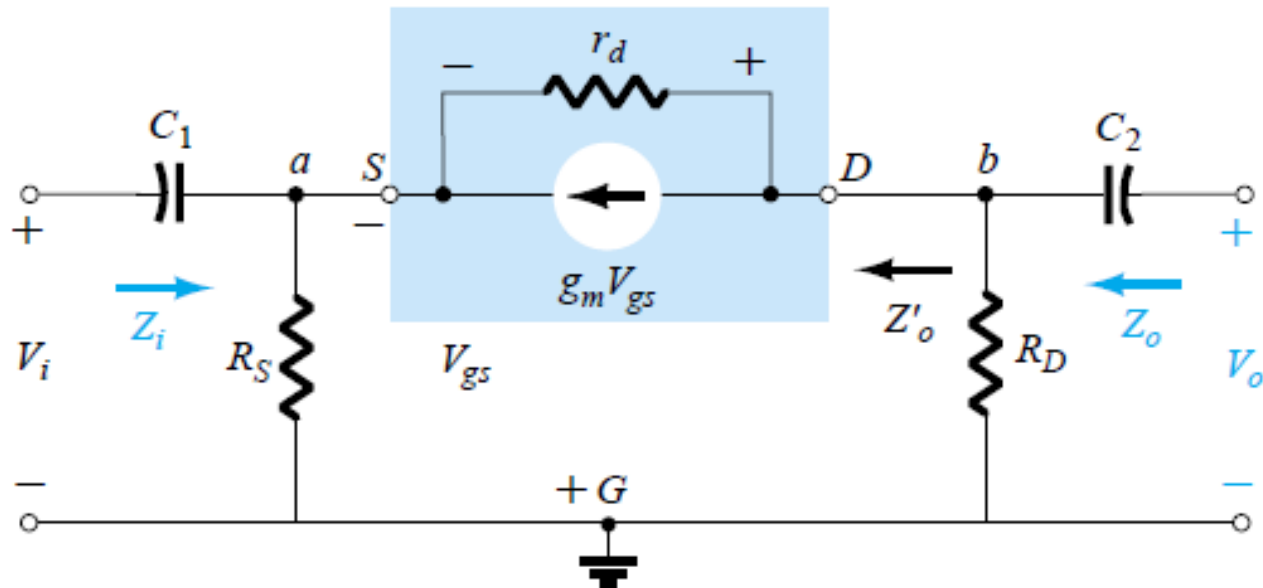 

 Z_i : The resistor R_S is directly across the terminals defining Z_i . Let us therefore find the impedance Z'_i which will simply be in parallel with R_S when Z_i is defined.



$$V' - V_{r_d} - V_{R_D} = 0$$

$$V_{r_d} = V' - V_{R_D} = V' - I'R_D$$

Applying Kirchhoff's current law at node a results in

$$I' + g_m V_{gs} = I_{r_d}$$

$$I' = I_{r_d} - g_m V_{gs} = \frac{(V' - I'R_D)}{r_d} - g_m V_{gs}$$

$$I' = \frac{V'}{r_d} - \frac{I'R_D}{r_d} - g_m[-V']$$

$$I' \left[1 + \frac{R_D}{r_d} \right] = V' \left[\frac{1}{r_d} + g_m \right]$$

$$Z'_i = \frac{V'}{I'} = \frac{\left[1 + \frac{R_D}{r_d} \right]}{\left[g_m + \frac{1}{r_d} \right]} = \frac{r_d + R_D}{1 + g_m r_d}$$

$$Z_i = R_S \parallel Z'_i$$

$$Z_i = R_S \parallel \left[\frac{r_d + R_D}{1 + g_m r_d} \right]$$

If $r_d \geq 10R_D$, and $1/r_d \ll g_m$:

$$Z'_i = \frac{\left[1 + \frac{R_D}{r_d} \right]}{\left[g_m + \frac{1}{r_d} \right]} \cong \frac{1}{g_m}$$

$$Z_i \cong R_S \parallel 1/g_m \quad r_d \geq 10R_D$$

Z_o : Substituting $V_i = 0$ V in will “short-out” the effects of R_S and set V_{gs} to 0 V. The result is $g_m V_{gs} = 0$, and r_d will be in parallel with R_D . Therefore,

$$Z_o = R_D \parallel r_d$$

For $r_d \geq 10R_D$,

$$Z_o \cong R_D$$

$r_d \geq 10R_D$

A_v :

$$V_i = -V_{gs}$$

and

$$V_o = I_D R_D$$

The voltage across r_d is

$$V_{r_d} = V_o - V_i$$

and

$$I_{r_d} = \frac{V_o - V_i}{r_d}$$

Applying Kirchhoff's current law at node b results in

$$I_{r_d} + I_D + g_m V_{gs} = 0$$

and

$$\begin{aligned} I_D &= -I_{r_d} - g_m V_{gs} \\ &= -\left[\frac{V_o - V_i}{r_d} \right] - g_m [-V_i] \\ I_D &= \frac{V_i - V_o}{r_d} + g_m V_i \end{aligned}$$

so that

$$\begin{aligned}V_o &= I_D R_D = \left[\frac{V_i - V_o}{r_d} + g_m V_i \right] R_D \\ &= \frac{V_i R_D}{r_d} - \frac{V_o R_D}{r_d} + g_m R_D\end{aligned}$$

and

$$V_o \left[1 + \frac{R_D}{r_d} \right] = V_i \left[\frac{R_D}{r_d} + g_m R_D \right]$$

with

$$A_v = \frac{V_o}{V_i} = \frac{\left[g_m R_D + \frac{R_D}{r_d} \right]}{\left[1 + \frac{R_D}{r_d} \right]}$$

For $r_d \geq 10R_D$,

$$A_v = g_m R_D$$


$r_d \geq 10R_D$

Phase Relationship: The fact that A_v is a positive number will result in an *in-phase* relationship between V_o and V_i for the common-gate configuration.

 Example 7

If $V_{GS_Q} = -2.2 \text{ V}$ and $I_{D_Q} = 2.03 \text{ mA}$:

- Determine g_m .
- Find r_d .
- Calculate Z_i with and without r_d . Compare results.
- Find Z_o with and without r_d . Compare results.
- Determine V_o with and without r_d . Compare results.




Solution

6. Depletion-Type MOSFETs Small Signal Model

The fact that Shockley's equation is also applicable to depletion-type MOSFETs results in the same equation for g_m . In fact, the ac equivalent model for D-MOSFETs is exactly the same as that employed for JFETs as shown in Fig. 9.33.


The only difference offered by D-MOSFETs is that V_{GS_Q} can be positive for n -channel devices and negative for p -channel units. The result is that g_m can be greater than g_{m0} as demonstrated by the example to follow. The range of r_d is very similar to that encountered for JFETs.

 

 Example 8



For the following circuit, if $V_{GS_Q} = 0.35 \text{ V}$ and $I_{D_Q} = 7.6 \text{ mA}$.

- Determine g_m and compare to g_{m0} .
- Find r_d .
- Sketch the ac equivalent network
- Find Z_i .
- Calculate Z_o .
- Find A_v .




Solution

TABLE 9.1 Z_i , Z_o , and A_v for various FET configurations

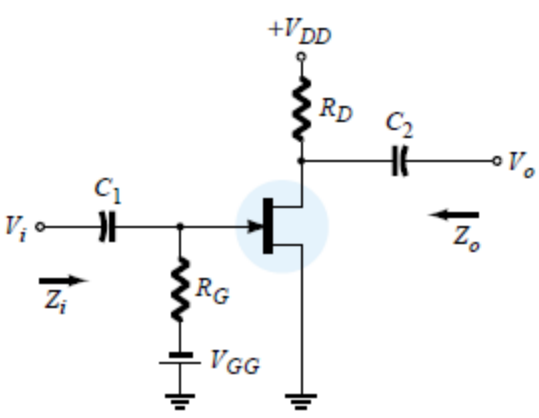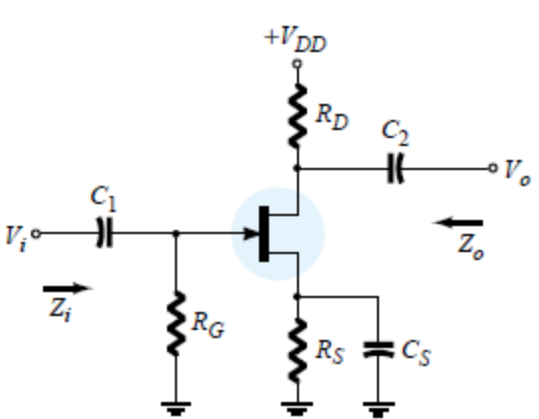Configuration	Z_i	Z_o	$A_v = \frac{V_o}{V_i}$
<p>Fixed-bias [JFET or D-MOSFET]</p> 	<p>High (10 MΩ) = R_G</p>	<p>Medium (2 kΩ) = $R_D r_d$ $\cong R_D$ ($r_d \geq 10 R_D$)</p>	<p>Medium (-10) = $-g_m(r_d R_D)$ $\cong -g_m R_D$ ($r_d \geq 10 R_D$)</p>
<p>Self-bias bypassed R_S [JFET or D-MOSFET]</p> 	<p>High (10 MΩ) = R_G</p>	<p>Medium (2 kΩ) = $R_D r_d$ $\cong R_D$ ($r_d \geq 10 R_D$)</p>	<p>Medium (-10) = $-g_m(r_d R_D)$ $\cong -g_m R_D$ ($r_d \geq 10 R_D$)</p>

 Self-bias
unbypassed R_S
[JFET or D-MOSFET]



High (10 M Ω)
= R_G

$$= \frac{\left[1 + g_m R_S + \frac{R_S}{r_d} \right] R_D}{\left[1 + g_m R_S + \frac{R_S}{r_d} + \frac{R_D}{r_d} \right]}$$


$$= R_D \quad [r_d \geq 10 R_D \text{ or } r_d = \infty \Omega]$$

Low (-2)

$$= \frac{g_m R_D}{1 + g_m R_S + \frac{R_D + R_S}{r_d}}$$

$$\cong \frac{g_m R_D}{1 + g_m R_S} \quad [r_d \geq 10(R_d + R_S)]$$

Voltage-divider bias
[JFET or D-MOSFET]

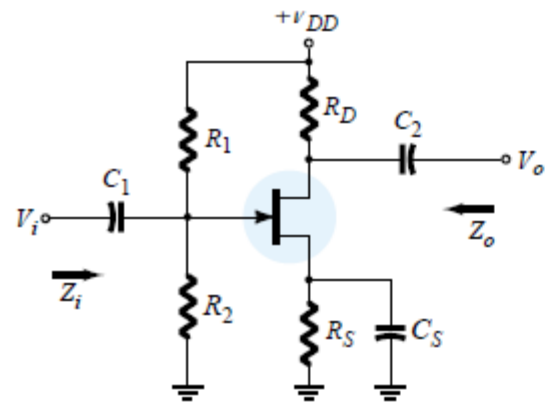

High (10 M Ω)
= $R_1 \parallel R_2$

Medium (2 k Ω)



$$= R_D \parallel r$$

$$\cong R_D \quad (r_d \geq 10 R_D)$$

Medium (-10)

$$= -g_m (r_d \parallel R_D)$$

$$\cong -g_m R_D \quad (r_d \geq 10 R_D)$$

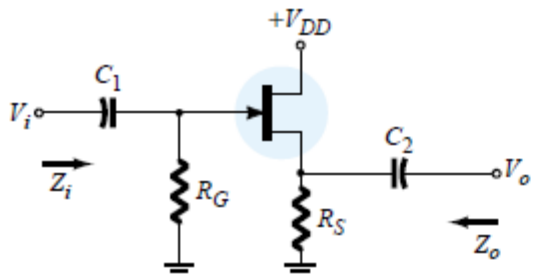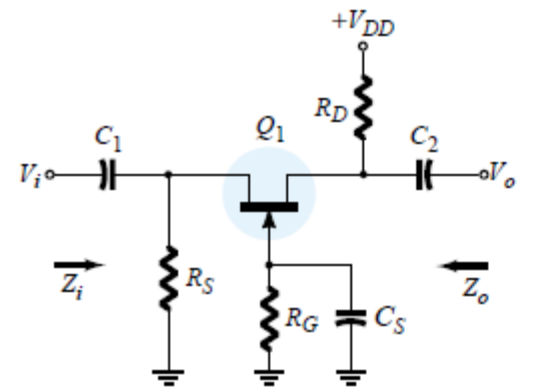Configuration	Z_i	Z_o	$A_v = \frac{V_o}{V_i}$
<p>Source-follower [JFET or D-MOSFET]</p> 	<p>High (10 MΩ)</p> $= R_G$	<p>Low (100 Ω)</p> $= r_d \parallel R_S \parallel 1/g_m$ $\cong R_S \parallel 1/g_m \quad (r_d \geq 10 R_S)$	<p>Low (< 1)</p> $= \frac{g_m(r_d \parallel R_S)}{1 + g_m(r_d \parallel R_S)}$ $\cong \frac{g_m R_S}{1 + g_m R_S} \quad (r_d \geq 10 R_S)$
<p>Common-gate [JFET or D-MOSFET]</p> 	<p>Low (1 kΩ)</p> $= R_S \parallel \left[\frac{r_d + R_D}{1 + g_m r_d} \right]$ $\cong R_S \parallel \frac{1}{g_m} \quad (r_d \geq 10 R_D)$	<p>Medium (2 kΩ)</p> $= R_D \parallel r_d$ $\cong R_D \quad (r_d \geq 10 R_D)$	<p>Medium (+10)</p> $= \frac{g_m R_D + \frac{R_D}{r_d}}{1 + \frac{R_D}{r_d}}$ $\cong g_m R_D \quad (r_d \geq 10 R_S)$

