

Example 1-7

Figure 1-9 shows the one-line diagram of simple three-bus power system with generation at bus 1. The magnitude of voltage at bus 1 is adjusted to 1.05 pu. The scheduled loads at bus 2 and 3 are marked on the diagram. Line impedances are marked in per unit on a 100 MVA base and the line charging susceptances are neglected.

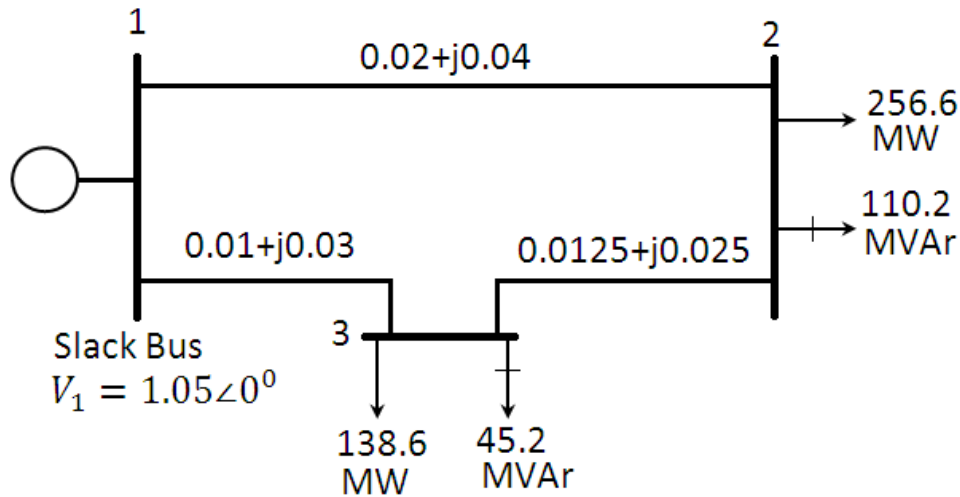


Figure (1-9) One-line diagram of Example 1-7 (impedances in pu on 100 MVA base)

- a) Using the Gauss-Seidel method, determine the phasorvalue of the voltage at the load buses 2 and 3 (P-Q buses) accurate to four decimal places.
- b) Find the slack bus real and reactive power.
- c) Determine the line flows and line losses. Construct a power flow diagram showing the direction of line flow.

(a) Line impedances are converted to admittances

$$y_{12} = \frac{1}{0.02 + j0.04} = 10 - j20$$

Similarly, $y_{13} = 10 - j30$, $y_{23} = 16 - j32$. The admittances are on the network shown in Figure 1-10.

At the P-Q buses, the complex lodes expressed in per units are

$$S_2^{sch} = -\frac{(256.6 + j110)}{100} = -2.566 - j1.102 pu$$

$$S_3^{sch} = -\frac{(138.6 + j45.2)}{100} = -1.386 - j0.452 \text{ pu}$$

Since the actual admittances are readily available in Figure 1-10, for hand calculation, we use (1-28). Bus 1 is taken as reference bus (slack). Starting from an initial estimate of

$$V_2^{(0)} = 1.0 + j0.0 \text{ and } V_3^{(0)} = 1.0 + j0.0,$$

V_2 and V_3 are computed from (1-28) as follows

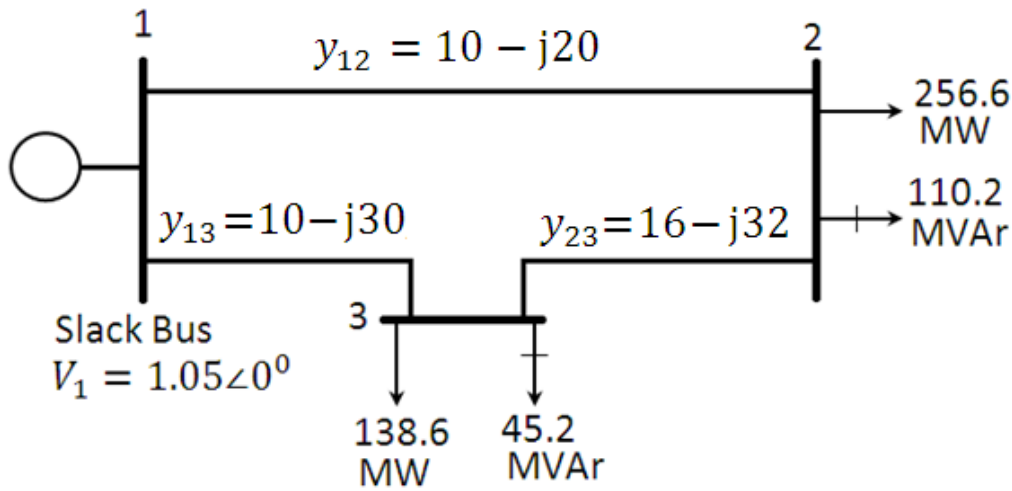


Figure (1-10) One-line diagram of Example 1-7 (admittances in pu on 100 MVA base)

$$V_2^{(1)} = \frac{\frac{P_2^{sch} - jQ_2^{sch}}{V_2^{*(0)}} + y_{12}V_1 + y_{23}V_3^{(0)}}{y_{12} + y_{23}}$$

$$V_2^{(1)} = \frac{\frac{-2.566 + j1.102}{1.0 - j0.0} + (10 - j20)(1.05 + j0.0) + (16 - j32)(1.0 + j0.0)}{(26 - j52)}$$

$$V_2^{(1)} = 0.9825 - j0.0310$$

and

$$V_3^{(1)} = \frac{\frac{P_3^{sch} - jQ_3^{sch}}{V_3^{*(0)}} + y_{13}V_1 + y_{23}V_2^{(1)}}{y_{13} + y_{23}}$$

$$V_3^{(1)} = \frac{\frac{-1.386 + j0.452}{1.0 - j0.0} + (10 - j30)(1.05 + j0.0) + (16 - j32)(0.9825 - j0.0310)}{(26 - j62)}$$

$$V_3^{(1)} = 1.0011 - j0.0353$$

For the second iteration we have

$$V_2^{(2)} = \frac{\frac{-2.566+j1.102}{0.9825+j0.0310} + (10 - j20)(1.05 + j0.0) + (16 - j32)(1.001 + j0.0353)}{(26 - j52)}$$

$$V_2^{(2)} = 0.9816 - j0.0520$$

and

$$V_3^{(2)} = \frac{\frac{-1.386+j0.452}{1.0011-j0.0353} + (10 - j30)(1.05 + j0.0) + (16 - j32)(0.9816 - j0.052)}{(26 - j62)}$$

$$V_3^{(2)} = 1.0008 - j0.0459$$

The process is continued and a solution is converted with an accuracy of 5×10^{-5} per unit as given below.

$$\begin{aligned} V_2^{(3)} &= 0.9808 - j0.0578, & V_3^{(3)} &= 1.0004 - j0.0488 \\ V_2^{(4)} &= 0.9803 - j0.0594, & V_3^{(4)} &= 1.0002 - j0.0497 \\ V_2^{(5)} &= 0.9801 - j0.0598, & V_3^{(5)} &= 1.0001 - j0.0499 \\ V_2^{(6)} &= 0.9801 - j0.0599, & V_3^{(6)} &= 1.0000 - j0.0500 \\ V_2^{(7)} &= 0.9800 - j0.0600, & V_3^{(7)} &= 1.0000 - j0.0500 \end{aligned}$$

The final solution is

$$V_2 = 0.9800 - j0.0600 = 0.98183 \angle -3.5035^\circ \text{ pu}$$

$$V_3 = 1.0000 - j0.0500 = 1.001125 \angle -2.8624^\circ \text{ pu}$$

(b) with the knowledge of all bus voltages, the slack bus powers is obtained from (1-27)

$$P_1 - jQ_1 = V_1^* [V_1(y_{12} + y_{13}) - (y_{12}V_2 + y_{13}V_3)]$$

$$P_1 - jQ_1 = 1.05[1.05(20 - j50) - (10 - j20)(0.98 - j0.06) - (10 - j30)(1.0 - j0.05)]$$

$$P_1 - jQ_1 = 4.095 - j1.98 \text{ pu}$$

or the slack bus real and reactive powers are

$$P_1 = 4.095 \text{ pu} = 409.5 \text{ MW}$$

$$Q_1 = 1.98 \text{ pu} = 189 \text{ MVar}$$

(b) To find the line flows, first the line current are computed. With line charging capacitors neglected, the line current are

$$I_{12} = y_{12}(V_1 - V_2) = (10 - j20)[(1.05 + j0) - (0.98 - j0.06)]$$

$$I_{12} = 1.9 - j0.8$$

$$I_{21} = -I_{12}$$

$$I_{13} = y_{13}(V_1 - V_3) = (10 - j30)[(1.05 + j0) - (1.0 - j0.05)]$$

$$I_{13} = 2.0 - j1.0$$

$$I_{31} = -I_{13} = -2.0 + j1.0$$

$$I_{23} = y_{23}(V_2 - V_3) = (16 - j32)[(0.98 - j0.06) - (1.0 - j0.05)]$$

$$I_{23} = -0.64 + j4.8$$

$$I_{32} = -I_{23} = 0.64 - j4.8$$

The line flows are

$$\begin{aligned} S_{12} &= V_1 I_{12}^* = (1.05 + j0.0)(1.9 + j0.8) = 1.995 + j0.84 \text{ pu} \\ &= 199.5 \text{ MW} + j84.0 \text{ Mvar} \end{aligned}$$

$$\begin{aligned} S_{21} &= V_2 I_{21}^* = (0.98 - j0.06)(-1.9 - j0.8) = -1.91 - j0.67 \text{ pu} \\ &= -191.0 \text{ MW} - j67.0 \text{ Mvar} \end{aligned}$$

$$\begin{aligned} S_{13} &= V_1 I_{13}^* = (1.05 + j0.0)(2.0 + j1.0) = 2.1 + j1.05 \text{ pu} \\ &= 210 \text{ MW} + j105.0 \text{ Mvar} \end{aligned}$$

$$\begin{aligned} S_{31} &= V_3 I_{31}^* = (1.0 + j0.05)(-2.0 - j1.0) = -2.05 - j0.90 \text{ pu} \\ &= -205.0 \text{ MW} - j90.0 \text{ Mvar} \end{aligned}$$

$$\begin{aligned} S_{23} &= V_2 I_{23}^* = (0.98 - j0.06)(-0.656 + j4.8) = -0.656 - j4.432 \text{ pu} \\ &= -65.6 \text{ MW} - j443.2 \text{ Mvar} \end{aligned}$$

$$\begin{aligned} S_{32} &= V_3 I_{32}^* = (1.0 - j0.05)(0.64 + j4.8) = 0.664 + j4.448 \text{ pu} \\ &= 66.4 \text{ MW} + j444.8 \text{ Mvar} \end{aligned}$$

and the line losses are

$$S_{\text{Los.12}} = S_{12} + S_{21} = 8.5 \text{ MW} + j17.0 \text{ Mvar}$$

$$S_{\text{Los.13}} = S_{13} + S_{31} = 5.0 \text{ MW} + j15.0 \text{ Mvar}$$

$$S_{\text{Los.23}} = S_{23} + S_{32} = 0.8 \text{ MW} + j1.60 \text{ Mvar}$$

The power flow diagram is shown in Figure 1-6, where real power direction is indicated by \rightarrow and the reactive power direction is indicated by $\rightarrow+$. The values within parentheses are the real and reactive losses in line.

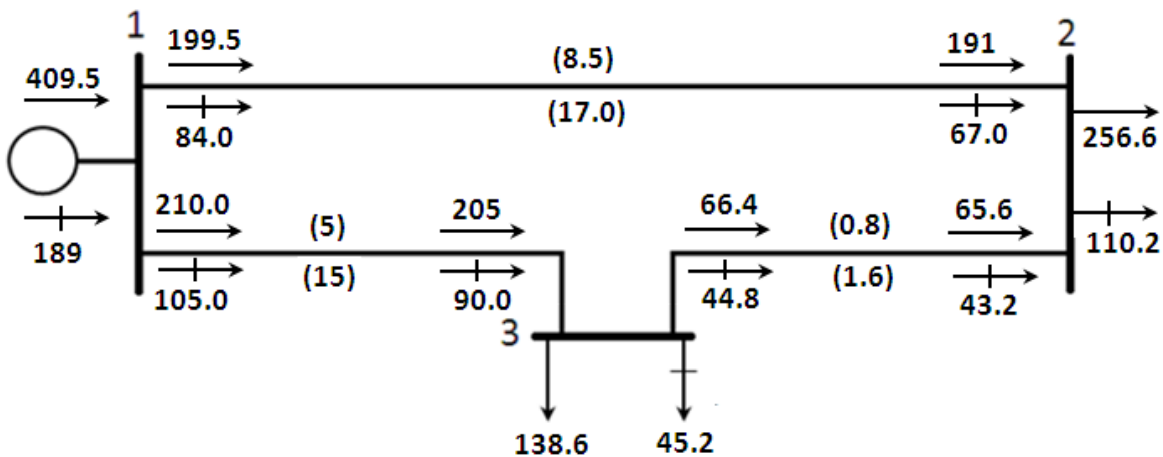


Figure (1-11) Power flow of Example 1-7 (powers in MW and MVAR)

Example 1-8

Figure 1-12 shows the one-line diagram of simple three-bus power system with generation at bus 1 and bus 2. Voltage magnitude at bus 3 is fixed at 1.04 pu with a real power generation of 200 MW. A load consisting of 400 MW and 250 MVar is taken from bus 2. Line impedances marked in per unit on a 100 MVA base, and the line charging susceptances are neglected. Obtain the power flow solution by the Gauss-Seidel method including line flows and line losses.

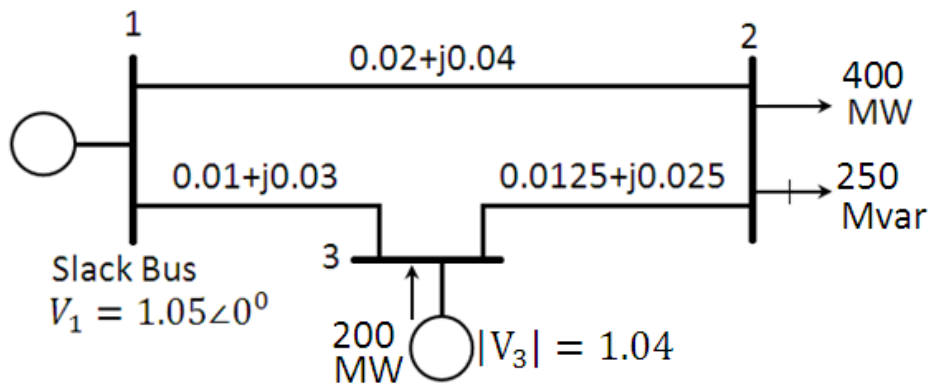


Figure (1-12) One-line diagram of Example 1-8 (impedances in pu on 100 MVA base)

(a) Line impedances are converted to admittances

$$y_{12} = \frac{1}{0.02 + j0.04} = 10 - j20$$

Similarly, $y_{13} = 10 - j30$, $y_{23} = 16 - j32$. The admittances are on the network shown in Figure 1-12b.

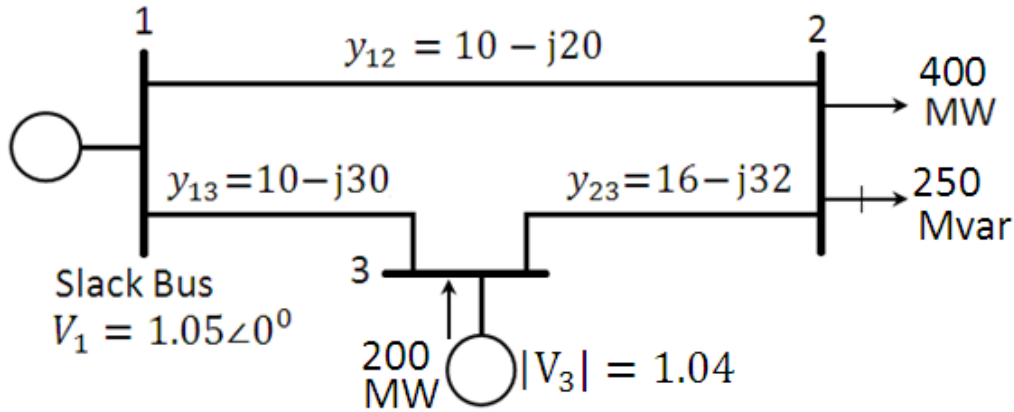


Figure (1-12b) One-line diagram of Example 1-7 (admittances in pu on 100 MVA base)

At the P-Q buses, the complex loads expressed in per units are

$$S_2^{sch} = -\frac{(400 + j250)}{100} = -4.0 - j2.5 \text{ pu}$$

$$P_3^{sch} = -\frac{200}{100} = 2.0 \text{ pu}$$

Bus 1 is taken as reference bus (slack bus). Starting from an initial estimate of $V_2^{(0)} = 1.0 + j0.0$ and $V_3^{(0)} = 1.04 + j0.0$,

V_2 and V_3 are computed from (1-28)

$V_i^{(k+1)} = \frac{\frac{P_i - jQ_i}{V_i^{*(k)}} + \sum_{j=0}^N y_{ij} V_j^k}{\sum_{j=0}^N y_{ij}} \quad j \neq i$	(1-28)
--	--------

$$V_2^{(1)} = \frac{\frac{P_2^{sch} - jQ_2^{sch}}{V_2^{*(0)}} + y_{12} V_1 + y_{23} V_3^{(0)}}{y_{12} + y_{23}}$$

$$V_2^{(1)} = \frac{\frac{-4.0 + j2.5}{1.0 - j0.0} + (10 - j20)(1.05 + j0.0) + (16 - j32)(1.04 + j0.0)}{(26 - j52)}$$

$$V_2^{(1)} = 0.97462 - j0.042307$$

Bus 3 is a regulated bus where voltage magnitude and real power are specified. For the **voltage-controlled bus, first the reactive power is computed from (1-30)**

$$P_i^{(k+1)} = \text{Re}\{V_i^{*(k)} [V_i^{(k)} \sum_{j=0}^N y_{ij} - \sum_{j=1}^N y_{ij} V_j^{(k)}]\} \quad j \neq i \quad (1-29)$$

$$Q_i^{(k+1)} = -\text{Im}\{V_i^{*(k)} [V_i^{(k)} \sum_{j=0}^N y_{ij} - \sum_{j=1}^N y_{ij} V_j^{(k)}]\} \quad j \neq i \quad (1-30)$$

$$Q_3^{(1)} = -\text{Im}\{V_3^{*(0)} [V_3^{(0)} (y_{13} + y_{23}) - y_{13} V_1 - y_{23} V_2^{(1)}]\}$$

$$Q_3^{(1)} = -\text{Im}\{(1.04-j0)[(1.04+j0)(26-j62)-(10-j30)(1.05+j0)-(16-j32)(0.97462-j0.042307)]\}$$

$$Q_3^{(1)} = 16$$

The value of $Q_3^{(1)}$ is used as Q_3^{sch} for the computation of voltage at bus 3. The complex voltage at bus 3, denoted by $V_{c3}^{(1)}$, is calculated

$$V_{c3}^{(1)} = \frac{\frac{P_3^{sch} - jQ_3^{sch}}{V_3^{*(0)}} + y_{13} V_1 + y_{23} V_2^{(1)}}{y_{13} + y_{23}}$$

$$V_{c3}^{(1)} = \frac{\frac{2.0-j1.16}{1.04-j0.0} + (10-j30)(1.05+j0.0) + (16-j32)(0.97462-j0.042307)}{(26-j62)}$$

$$V_{c3}^{(1)} = 1.03783 - j0.005170$$

Since $|V_3|$ is held constant at 1.04 pu, only the imaginary part of $V_{c3}^{(1)}$ is retained, i.e. $f_3^{(1)} = -0.005170$, and its real part is obtained from

$$e_3^{(1)} = \sqrt{(1.04)^2 - (0.005170)^2} = 1.039987$$

Thus

$$V_3^{(1)} = 1.039987 - j0.005170$$

For the second iteration, we have

$$V_2^{(2)} = \frac{\frac{P_2^{sch} - jQ_2^{sch}}{V_2^{*(1)}} + y_{12} V_1 + y_{23} V_3^{(1)}}{y_{12} + y_{23}}$$

$$V_2^{(2)} = \frac{\frac{P_2^{sch} - jQ_2^{sch}}{V_2^{*(1)}} + y_{12}V_1 + y_{23}V_3^{(1)}}{y_{12} + y_{23}}$$

$$V_2^{(2)} = \frac{\frac{-4.0 + j2.5}{0.97462 - j0.042307} + (10 - j20)(1.05) + (16 - j32)(1.039987 - j0.005170)}{(26 - j52)}$$

$$V_2^{(2)} = 0.971057 - j0.043432$$

$$Q_3^{(2)} = -Im\{V_3^{*(1)}[V_3^{(1)}(y_{13} + y_{23}) - y_{13}V_1 - y_{23}V_2^{(2)}]\}$$

$$Q_3^{(2)} = -Im\{(1.039987 - j0.005170)[(1.039987 - j0.005170)(26 - j62) - (10 - j30)(1.05 + j0) - (16 - j32)(0.971057 - j0.043432)]\}$$

$$Q_3^{(2)} = 1.38796$$

$$V_{c3}^{(2)} = \frac{\frac{P_3^{sch} - jQ_3^{sch}}{V_3^{*(1)}} + y_{13}V_1 + y_{23}V_2^{(2)}}{y_{13} + y_{23}}$$

$$V_{c3}^{(2)} = \frac{\frac{2.0 - j1.38796}{1.039987 + j0.005170} + (10 - j30)(1.05) + (16 - j32)(0.971057 - j0.043432)}{(26 - j62)}$$

$$V_{c3}^{(2)} = 1.03908 - j0.00730$$

Since $|V_3|$ is held constant at 1.04 pu, only the imaginary part of $V_{c3}^{(2)}$ is retained, i.e. $f_3^{(2)} = -0.00730$, and its real part is obtained from

$$e_3^{(2)} = \sqrt{(1.04)^2 - (0.00730)^2} = 1.039974$$

or

$$V_3^{(2)} = 1.0399974 - j0.00730$$

The process is continued and a solution is converged with an accuracy of 5×10^{-5} per unit in seven iterations as given below.

$$V_2^{(3)} = 0.97073 - j0.04479, \quad Q_3^{(3)} = 1.42904, \quad V_3^{(3)} = 1.03996 - j0.00833$$

$$V_2^{(4)} = 0.97065 - j0.04533, \quad Q_3^{(4)} = 1.44833, \quad V_3^{(4)} = 1.03996 - j0.00873$$

$$V_2^{(5)} = 0.97062 - j0.04555, \quad Q_3^{(5)} = 1.45621, \quad V_3^{(5)} = 1.03996 - j0.00893$$

$$V_2^{(6)} = 0.97061 - j0.04565, \quad Q_3^{(6)} = 1.45947, \quad V_3^{(6)} = 1.03996 - j0.00900$$

$$V_2^{(7)} = 0.97061 - j0.04569, Q_3^{(7)} = 1.46082 V_3^{(7)} = 1.03996 - j0.00903$$

The final solution is

$$V_2 = 0.97168 \angle -2.6948^\circ \text{ pu}$$

$$S_3 = 2.0 + j1.4617 \text{ pu}$$

$$V_3 = 1.04 \angle -0.498^\circ \text{ pu}$$

with the knowledge of all bus voltages, the slack bus powers is obtained from (1-27)

$\frac{P_i - jQ_i}{V_i^*} = V_i \sum_{j=0}^N y_{ij} - \sum_{j=1}^N y_{ij} V_j \quad j \neq i$	(1-27)
---	--------

$$P_1 - jQ_1 = V_1^* [V_1(y_{12} + y_{13}) - (y_{12}V_2 + y_{13}V_3)]$$

$$S_1 = 2.1842 + j1.4085 \text{ pu}$$

Line flow and line losses are computed and the result expressed in **MW and MVar**

$$S_{12} = 179.36 + j118.734, \quad S_{21} = -170.97 - j101.947$$

$$S_{13} = 39.06 + j22.118, \quad S_{31} = -38.88 + j21.569$$

$$S_{23} = -229.03 - j148.05, \quad S_{32} = 238.88 + j167.746$$

$$S_{Los.12} = S_{12} + S_{21} = 8.39 + j16.79$$

$$S_{Los.13} = S_{13} + S_{31} = 0.18 + j0.548$$

$$S_{Los.23} = S_{23} + S_{32} = 9.85 + j19.69$$